647510

0303212C3030

Seat No: _____

B.Sc.(IT) Semester - 2 (CBCS) Examination March/April- 2018 COMPUTER ORGANIZATION & ARCHITECTURE

(CORE)

Time: 2:30 Hours Instructions: 1. All questions are compulsory. 2. Figures to the right indicate marks. Que-1 (A) Attempt following questions. (1) In full-adder, there are three input and output terminal. (2) A gate is a logic circuit with one or more input signals but output signal. (3) A sign is used to show the AND operation. (4) In JK flip flop, JK stands for Que-1 (B) Attempt following.(Attempt any one) (1) What is logic gate? (2) What is sequential circuit? Que-1 (C) Attempt following.(Attempt any one) (1) Explain half Adder. (2) Explain De-Morgan's theorems. Que-1 (D) Attempt following.(Attempt any one) (1) Explain SR flip flop in detail. (2) Write a note on Full Adder. Que-2 (A) Attempt following questions. (1) VLSI stands for (2) DIL stands for (3) PISO stands for (4) Multiplexing means into one. Que-2 (B) Attempt following.(Attempt any one) (1) What is IC? (2) List applications of shift register. Que-2 (C) Attempt following.(Attempt any one) (1) Explain block diagram of Register. (2) Explain Octal to Binary encoder. Que-2 (D) Attempt following.(Attempt any one) (1) Explain asynchronous 4 bit binary counters. (2) Write a note on 4 * 1 Multiplexer.		larks: 70	
2. Figu	ures to		
Que-1	(A)	Attempt following questions.	(04)
			, ,
			ıal.
		•	
0 1	(D)	August 6-11	(02)
Que-1	` ′		(02)
	(2)	what is sequential circuit?	
Que-1	(C)	Attempt following.(Attempt any one)	(03)
	(1)	Explain half Adder.	
	(2)	Explain De-Morgan's theorems.	
Oue-1	(D)	Attempt following (Attempt any one)	(05)
Quc-1			(03)
		* * *	
	(2)	write a note on run Adder.	
Que-2	(A)		(04)
	(1)	VLSI stands for	
	(2)		
	(3)	PISO stands for	
	(4)	Multiplexing means into one.	
Oue-2	(B)	Attempt following (Attempt any one)	(02)
Q			(02)
	(2)	List applications of shift register.	
Que-2	(C)	Attempt following.(Attempt any one)	(03)
	(1)	Explain block diagram of Register.	
	(2)		
Que-2			(05)
	(1)	1 7	
	(2)	Write a note on 4 * 1 Multiplexer.	
Que-3	(A)	To calculate following binary digits.	(04)
<u></u>	(1)	110 * 110 =	(= -)
	(2)	1010.1 * 110 =	
	(3)	10000111/101 =	
	(4)	110000111/1011 =	

Que-3	(B) (1) (2)	Attempt following.(Attempt any one) Explain rules of binary Addition. Explain rules of binary Subtraction.	(02)
Que-3	(C) (1) (2)	Attempt following.(Attempt any one) Explain floating point representation of number. Explain 2's complement method in detail with example.	(03)
Que-3	(D) (1) (2)	Attempt following.(Attempt any one) Explain error detection code. Write note on Parity bit.	(05)
Que-4	(A) (1) (2) (3) (4)	Attempt following questions. RPN stands for perform arithmetic and logical calculation. The process of inserting an item into the stack is known as In notation the operator is placed before the operand.	(04)
Que-4	(B) (1) (2)	Attempt following.(Attempt any one) What is Stack? Explain Advantages of Polish Notation.	(02)
Que-4	(C) (1) (2)	Attempt following.(Attempt any one) Explain Micro Operation. Write a short note on ALU.	(03)
Que-4	(D) (1) (2)	Attempt following.(Attempt any one) What is RPN? Explain use of RPN using stack with suitable example. What is Interrupt explain in detail with types.	(05)
Que-5	(A) (1) (2) (3) (4)	Attempt following questions. IOP stands for DMA stands for is a bidirectional bus which allows the transfer of data between the microprocessor and memory or peripheral device. carries address of memory location or port number of peripherals device.	(04)
Que-5	(B) (1) (2)	Attempt following.(Attempt any one) List out Registers of DMA controller. What is DMA?	(02)
Que-5	(C) (1) (2)	Attempt following.(Attempt any one) Explain Address register and word-count register in detail. Explain Memory bus.	(03)
Que-5	(D) (1) (2)	Attempt following.(Attempt any one) Explain DMA Transfer in detail. Explain IOP in detail.	(05)
